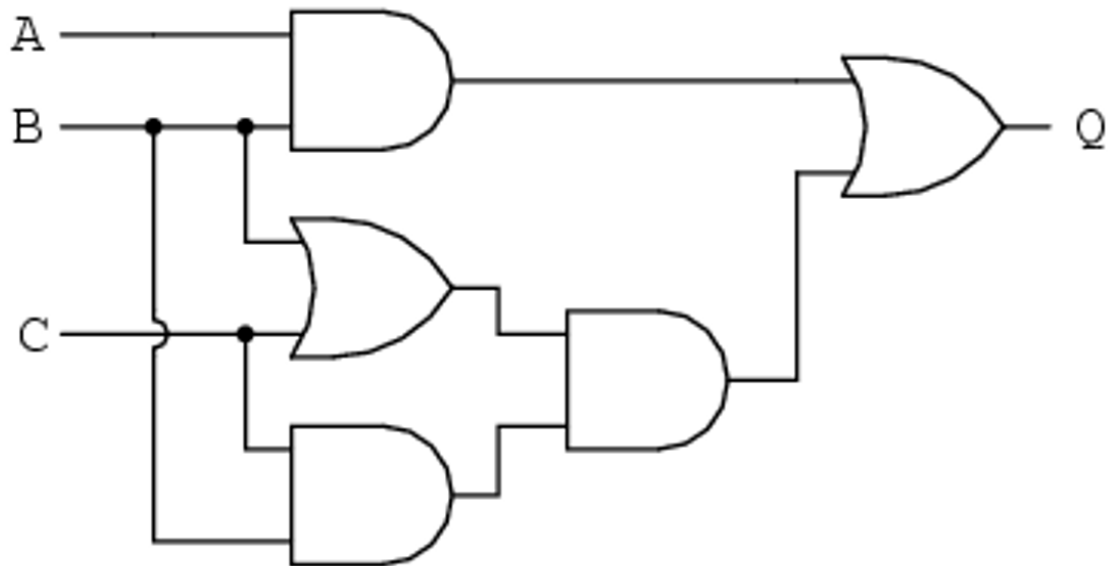


Circuit simplification Example



Step 1: Write a Boolean expression for the circuit.

Step 2: Use Boolean simplification to reduce this expression.